

COUNTER CIRCUIT

Computer Technology
TEJ20
Grade 10
June 2020



**ONLINE
RESOURCE**



Table of Contents

Introduction	2
Project Outline.....	2
Prior Knowledge.....	2
Student Activities.....	2
Activity 1 – Intro to Electronics.....	2
Activity 2 – Introduction to Breadboarding	3
Activity 3 – Intro to Boolean Logic and Integrated Circuit Chips	4
Activity 4 – 555 Timer Circuit	5
Activity 5 – Seven Segment Display and Decoder Chip	5
Activity 6 – Counter Circuit Project	7
Instructional Strategies.....	7
The Hook / Motivational Strategies	7
Overall and Specific Expectations.....	8
Overall Expectations.....	8
Specific Expectations.....	8
Safety Concerns (including PPE if required)	8
Applicable SAFEDocs and ToolSAFE videos.....	8
Differentiation of the Project / Activity.....	9
Assessment and Evaluation	9
Reflection	9
Appendix A – Instructions for Using Classes on Tinkercad	10
Appendix B – Activity 1 Resources - Intro to Electronics.....	13
Activity 1: Introduction to Electronics – Completed Note	13
Activity 1: Introduction to Electronics – TEJ2O Student Note	14
Appendix C – Activity 2 Resources – Intro to Breadboarding.....	15
Section A: Create Basic Circuits on a Breadboard	16
Section B: Draw the Circuit Schematics for Circuits in Section A	17
Appendix D – Activity 3 Resources - Intro to Boolean Logic and Integrated Circuit Chips	18
Boolean Logic – TEJ2O Student Note and Worksheet.....	20
Basic Logic IC Chip Layouts – TEJ2O Student Note.....	23
Experimenting with Logic Gates on Logic.ly – TEJ2O	24
Integrated Circuits: Tinkercad Activity.....	25

Integrated Circuits: Tinkercad Activity Worksheet	26
Extension: Advanced Circuit	28
Logic Gates and Integrated Circuits - TEJ2O Quiz	29
Appendix E – Activity 4 Resources – 555 Timer Circuit	31
Building a 555 Timer Circuit – TEJ2O.....	31
Pinout for 555 Chip	33
Appendix F – Activity 5 Resources – Seven Segment Display and Decoder Chip	34
Labelled 7 Segment Pinout for teacher.....	34
Exploring a 7 Segment Display and Decoder Chip – TEJ2O	35
Appendix G – Activity 6 Resources – Counter Circuit Project	38
Activity #6 Building a Counter Circuit – TEJ2O.....	38
Counter Circuit Project Solutions	40
References.....	41

Introduction

Course Code: TEJ2O
Broad base Technology: Computer Technology
Destination: Workplace/ College / University
Grade Level: 10
Prerequisite: None
Online Project Name: Counter Circuit

Project Outline

The goal of this project is to build a counter circuit with a breadboard and various Integrated Circuit Chips which can be done in class (part list will be provided) or online with TinkerCAD (Autodesk's Web Based Simulator). The counter circuit will only use electronic devices to help students focus on wiring and troubleshooting circuits. Throughout the module activities students will learn about a variety of electronic devices (resistors, LEDs, capacitors, breadboards, Boolean logic chips, 555 Timer chip, and the 7 segment display and decoder chips).

Prior Knowledge

This project assumes no prior knowledge but there will be some basic electronics/electricity concepts they may have learned in Grade 9 science.

Student Activities

Activity 1 – Intro to Electronics

The goal of this activity is to introduce students to basic electronic components that can be used in electronics projects and activities. Students will be able to identify the components, schematic symbols, and describe the functions of the components.

Time required: 30 minutes

Materials/Equipment required if in class: resistors, wires, LEDs, capacitors, diodes, DIP Switch, buttons, breadboard, power supply, etc. for in class experiential learning. Teachers can also use the Tinkercad.com simulator and projector to introduce these items. The teacher should also draw some basic circuits to show schematic symbols. (i.e.: battery, buttons, resistor, and LED)

Resources: Teacher can use the [student handout](#) (Appendix B) as a guide for providing important details for basic components. The completed [example](#) has been included to support the teacher as well.

Activity 2 – Introduction to Breadboarding


The goal of this activity is to build some basic breadboard circuits using the components introduced in activity #1. The teacher will need to introduce the Tinkercad.com platform. Teachers are encouraged to explore the “Class” feature of [Tinkercad.com](#) ([See Appendix A – Instructions for Using Classes on Tinkercad](#)). It will allow the teacher to remotely view students’ circuits they build making it easier to provide detailed feedback on their work using any school board’s messaging platform.

Time required: 45 minutes

Materials/Equipment required if in class: Breadboards kits with power supplies, resistors (ideally a few different values – 220 Ohm, 1K Ohm, 10K Ohm, etc.), male to male jumper wires, LEDs, and buttons. Teacher can also use the Tinkercad.com simulator and projector to introduce these circuits. Try to avoid giving the students a power cable at first and have them come to you or you go around to them to test their first set of circuits.

Resources: The video lesson “TEJ2O A2 - Introduction to Breadboards and Basic Circuits on Tinkercad” is provided to give a basic overview of the Tinkercad Simulator and how to use breadboards and basic components. A [Student Activity Sheet](#) is also provided to accompany the video.

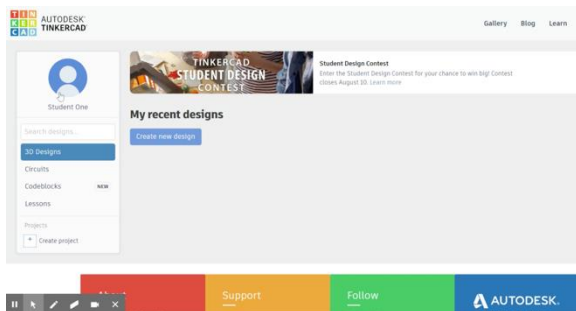Web link: Video – [Introduction to Breadboards and Basic Circuits on Tinkercad](#)



[https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2 - Introduction to Breadboards and Basic Circuits on Tinkercad.mp4](https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2_-_Introduction_to_Breadboards_and_Basic_Circuits_on_Tinkercad.mp4)

Assessment and Evaluation: Students should complete the activity sheet and the teacher can provide feedback on their circuits for formative assessment.

Activity 3 – Intro to Boolean Logic and Integrated Circuit Chips

The goal of this activity is to explore the six basic Boolean Logic operators (AND, OR, NOT, NAND, NOR, XOR) and the associated integrated circuit chips. Students will learn the theory behind Boolean Algebra (Logic) and will test these concepts with integrated circuit chips, breadboards, wires, LEDs, and resistors. There will be an opportunity for scaffolding and enrichment activities.


Time required: 120 minutes

Materials/Equipment Required in class: Breadboard kits with power supplies, resistors, male to male jumper wires, LEDs, and the following integrated circuit chips (74HC08, 74HC32, 74HC04, 74HC00, 74HC02, and 74HC86). The teacher can also use the Tinkercad.com simulator and projector to introduce these circuit chips. Avoid giving the students a power cable at first and have them come to you or you go around to them to test their first set of circuits to avoid damaging chips.

Resources:


- [Intro to Boolean Logic](#) (Teacher PowerPoint Presentation)
- [Intro to Boolean Logic](#) (Student Note and Worksheet)
- [Intro to Logic Chips Exploration Activity](#) (Teacher PowerPoint Presentation)
- [Basic Logic IC Chip Layouts](#) (Student Note and Worksheet)
- [LogicLY Boolean Assignment](#) (Scaffolding Activity)
- [Integrated Circuits on Tinkercad Activity](#) (Student Worksheet)
- [Logic Gates and Integrated Circuits Quiz](#)
- Introduction to Breadboards and Basic Circuits on Tinkercad (Video Activity)
- AND Integrated Circuit on Tinkercad (Video Activity)

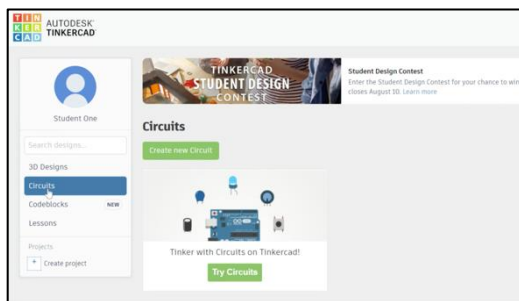Web link: Video – [Introduction to Breadboards and Basic Circuits on Tinkercad](#)



https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2_-_Introduction_to_Breadboards_and_Basic_Circuits_on_Tinkercad.mp4

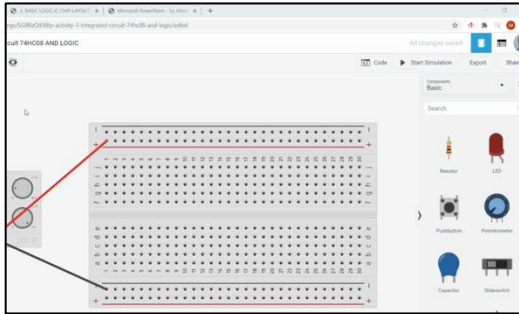Web link: Video – [AND Integrated Circuit on Tinkercad](#)



[https://www.octe.ca/application/files/5515/9624/2225/TEJ2O_A3 - AND Integrated Circuit on Tinkercad.mp4](https://www.octe.ca/application/files/5515/9624/2225/TEJ2O_A3_-_AND_Integrated_Circuit_on_Tinkercad.mp4)

Assessment and Evaluation: Students will complete a topic quiz.

Activity 4 – 555 Timer Circuit

The goal of this activity is to continue exploring electronics components and introducing the 555 Timer integrated circuit chip, capacitors, how resistor values affect the circuit, and how electronic components (not code) can keep track of time.

Time required: 30 minutes

Materials/Equipment required in class: Breadboards kits with power supplies, resistors (2K, 10K, 100K, 560K, 1.5M), male to male jumper wires, LEDs, 555 Timer Chip, and a capacitor (2.2uF). The teacher can also use the Tinkercad.com simulator and projector to introduce these circuit chips.

Resources: A student [activity sheet](#) is provided.

Assessment and Evaluation: Students will complete a circuit activity and submit their completed circuit to their teacher (through a Tinkercad class or image). The teacher will provide feedback and suggestions for troubleshooting.

Activity 5 – Seven Segment Display and Decoder Chip


The goal of this activity is to explore seven segment displays (digital number readout similar to an alarm clock), CD4511 seven segment decoder integrated circuit chip, capacitors, how resistor values affect the circuit, and how electronic components (not code) can keep track of time. The idea of common cathode vs. common anode will be introduced. The Binary number system will be reviewed to understand how a 4 digit binary number can produce a decimal value on the seven segment display.

Time required: 45 minutes

Materials/Equipment required in class: Breadboards kits with power supplies, resistor, male to male jumper wires, seven segment display (example: MAN72A) and decoder chip (example: 7447). The teacher can also use the Tinkercad.com simulator and projector to introduce these circuit chips.


Resources: A student [activity sheet](#) is provided. There are also two instructional videos provided.

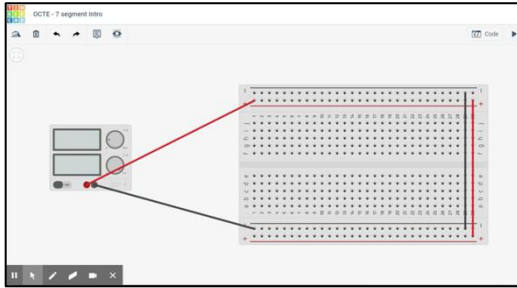Web link: Video – [7 Segment Intro on Tinkercad](#)



[https://www.octe.ca/application/files/3515/9624/2309/TEJ2O_A5a - 7 Segment Intro on Tinkercad.mp4](https://www.octe.ca/application/files/3515/9624/2309/TEJ2O_A5a_-_7_Segment_Intro_on_Tinkercad.mp4)

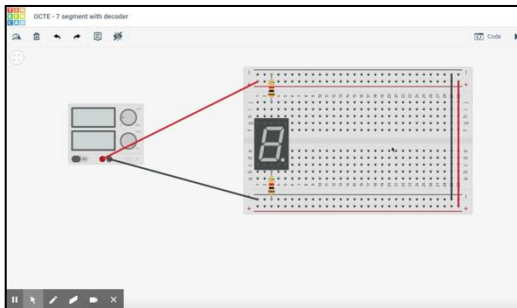Web link: Video – [7 segment with decoder on Tinkercad](#)



[https://www.octe.ca/application/files/6715/9624/2418/TEJ2O_A5b - 7 segment with decoder on Tinkercad.mp4](https://www.octe.ca/application/files/6715/9624/2418/TEJ2O_A5b_-_7_segment_with_decoder_on_Tinkercad.mp4)

Assessment and Evaluation: Students will complete a circuit activity and submit their completed circuit to their teacher (through Tinkercad class or image). The teacher will provide feedback and suggestions for troubleshooting.

Activity 6 – Counter Circuit Project

The goal of this activity is to combine the learning from previous activities to make a Counter Circuit. The student will have the option to create one of the following (or both as enrichment):

OPTION 1: Automated Counter Circuit using 555 Timer

OPTION 2: Button Driven Counter Circuit

Both options will require students to build a complex circuit with a new integrated circuit chip (74HC93). They will use previous feedback and activities to troubleshoot and build the circuit of their choice.

Time required: 60 minutes

Materials/Equipment required in class: Breadboards kits with power supplies, resistors (220, 2K, 1.5M), male to male jumper wires, seven segment display (example: MAN72A) and decoder chip (example: 7447), 2 buttons, 555 timer, capacitor (2.2 uF). The teacher can also use the Tinkercad.com simulator and projector to introduce these circuit chips.

Resources: A student [activity sheet](#) is provided.

Assessment and Evaluation: Students will complete a Counter Circuit and the teacher will evaluate the submitted circuit with the provided rubric. Students will also complete a KWL Chart (Knew/Wanted/Learned) and a Troubleshooting Log.

Instructional Strategies

Students can complete all of the activities from home with teacher support. There are a variety of lessons, exploratory activities, and tasks that can be completed from home using an online simulator. All activities (lessons, assignments, quizzes, etc.) can be easily completed and shared through an online learning system. Students can also submit all work done on the simulator online by “sharing” an image of their circuit. Instructions for teachers have been provided to setup a class on the Tinkercad website. Teachers can view live versions of students’ circuits and can complete assessment and evaluations by observing their work through the website.

The Hook / Motivational Strategies

Students will really enjoy building these circuits online as they can safely build, test, and troubleshoot their circuits with immediate feedback in the simulator.

Overall and Specific Expectations in Support of Ontario Curriculum Grades 9 - 10 Technological Education

Overall Expectations

A1. Identify and describe the functions of, as well as important advances related to, electronic and computer components;

A3. Demonstrate a basic understanding of binary numbers and digital logic.

B2. Construct and test simple interfaces and other electronic circuits;

Specific Expectations

A1.1 Identify basic electronic components and describe their functions (e.g., resistors limit current; capacitors store charge, pass high frequencies, and block DC; diodes restrict current in one direction; LEDs indicate current flow; transistors act as amplifiers or switches);

A3.3 Derive the truth tables of the fundamental logic gates (e.g., AND, OR, NOT, NOR, NAND, XOR);

A3.4 Write Boolean equations for the fundamental logic gates (e.g., for AND, the output is $Y = A \cdot B$; for OR, $Y = A + B$).

B2.1 Safely construct and test electronic circuits (e.g., LED circuit, flasher, timer), using both breadboard and soldering techniques to connect discrete components and/or integrated circuits;

Safety Concerns

All hands on work can be completed with an online simulator so there is little concern for safety. If activities are completed in class, the concerns may include overheating components that aren't wired properly. Teachers should supervise actively and encourage students to use safety glasses.

Applicable SAFEDocs and ToolSAFE videos

Please refer to the [Computer Technology SAFEDocs](#) located on the OCTE website.

Differentiation of the Project / Activity

Many supporting documents for students and teachers have been provided to ensure all types of learners are given the supports they need. All circuit activities are provided with graphical guides to follow and major concepts have corresponding video lessons with screen capture instructions.

Assessment and Evaluation

Assessment For Learning

Students will be given descriptive feedback for the variety of circuit activities they complete

Assessment Of Learning

1. [Logic Gate and Integrated Circuits Quiz](#)
2. [Rubric used for Final Counter Circuit](#)

Reflection


Teachers may wish to have the students complete a trouble shooting log and reflection to consolidate their learning. This would be a nice way to capture the student's understanding in a summative format and be used in preparation for their examination, entering post-secondary education or to the workforce.

Appendix A – Instructions for Using Classes on Tinkercad


Step 1: Click on “Classes”



Step 2: Create a New class by choosing a name, grade, and subject

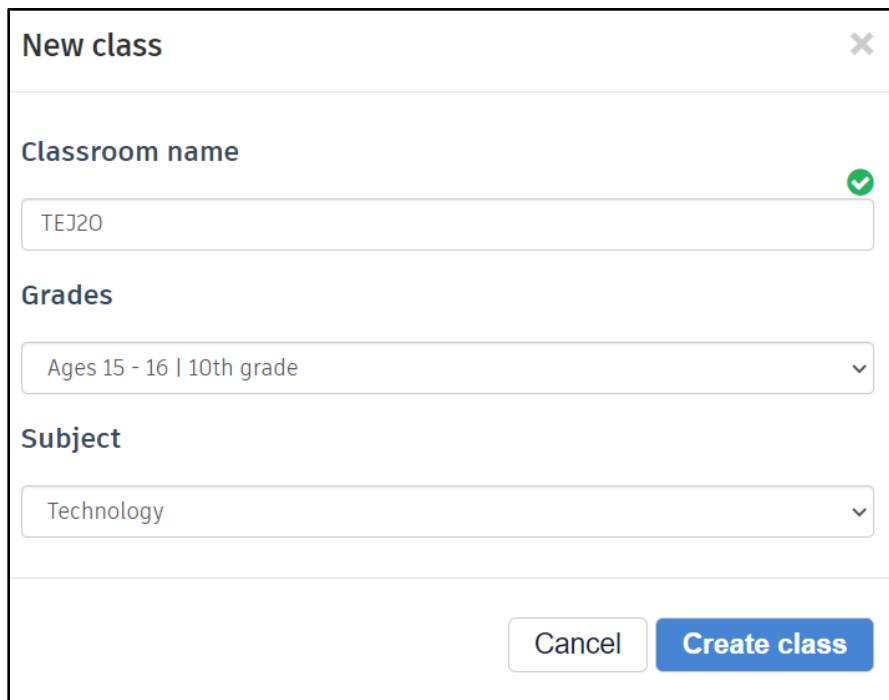A screenshot of the 'New class' form in Tinkercad. The form has a title 'New class' and a close button (X). It contains three input fields: 'Classroom name' with the value 'TEJ20' and a green checkmark; 'Grades' with the value 'Ages 15 - 16 | 10th grade'; and 'Subject' with the value 'Technology'. At the bottom, there are two buttons: 'Cancel' and 'Create class'.

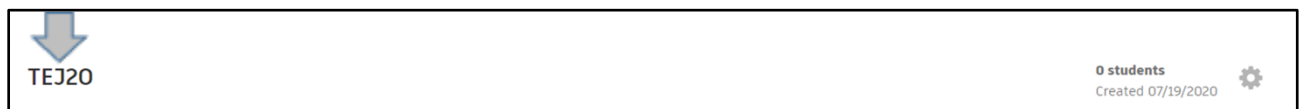Step 3: Click on the newly created class to add students/users




Step 4: Adding Students, you can add one student at a time OR click “Paste a list of students”.

Add students

Class: TEJ20

Name	Nickname	
<input type="text" value="For example: Amy Zeebo"/>	<input type="text" value="AmyZ56"/>	<input type="button" value="Save Changes"/>

Nickname must be 3 or more characters, numbers, or letters.




Step 5: Type or Copy the names of students then click “Add # students”.

Add students

Class: TEJ20

Student names

Student One
Student Two
Student Three
Student Four



Step 6: Give each student a unique nickname. This past year I used last name and first initial. Example: Bill Gates would be “gatesb” to make it easy to inform all students.





<input type="checkbox"/> Student name	Nickname
<input type="checkbox"/>  Student One	<input type="text" value="ones"/> 
<input type="checkbox"/>  Student Two	<input type="text" value="twos"/> 

Step 7: Now you will need to share the “Class Code” with your students.

< TEJ20 ×

Students Designs

Select action ▾ Add students **Class Code**

<input type="checkbox"/> Student name	Nickname
<input type="checkbox"/>  Student One	ones 
<input type="checkbox"/>  Student Two	twos 

Step 8: Use the given class code and share the join link to your students.

Log in to TEJ20 with:

TPI6 29LS DHMR

Student Instructions

Have a class link?

1. Go to your class at <https://www.tinkercad.com/joinclass/TPI629LSDHMR>.
2. Enter the **Nickname** your teacher assigned you.

Have a class code?

1. Go to <https://www.tinkercad.com/joinclass>
2. Enter your class code: **TPI629LSDHMR**
3. Enter the **Nickname** your teacher assigned you.

Appendix B – Activity 1 Resources - Intro to Electronics


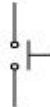
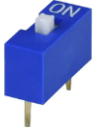
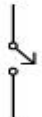



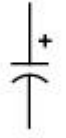



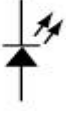
Activity 1: Introduction to Electronics – Completed Note

Electricity Basics

Name	Description (point form)	Unit of Measurement
Voltage	<ul style="list-style-type: none"> the force motivating electrons to flow considered the potential energy in the circuit you need to refer to two points to calculate voltage 	Volts
Current	<ul style="list-style-type: none"> how much charge is in a circuit during a given time the current produced by the flow of one coulomb per second 	Amps
Resistance	<ul style="list-style-type: none"> this refers to the opposition of flow of electrons again, this must be related to two points in a circuit 	Ohms (Ω)

Electronics Components

Below are some items and symbols that will be important for working with electronics.

Component Picture	Draw Schematic	Component Name	Brief Description
		Push Button (can be normally open or normally closed) *Teacher should show examples of each	This button needs to be pushed to allow flow in circuit.
		Switch	ON / OFF Switch flows while ON, no flow when OFF.
		Resistor	Slows the follow of current in a circuit (which also lowers voltage based on Ohm's law).
		Capacitor (polarized capacitor)	Temporarily stores electric charge. It acts like a bucket (with a hole in the bottom)...it fills then dumps the full amount. If not "filled" the electrons will drain.
		Diode	Only allows flow in one direction (with arrow). Can compare to a plumbing check valve.
		Light Emitting Diode (LED)	Only allows flow in one direction and also gives off light


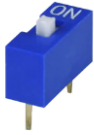




Activity 1: Introduction to Electronics – TEJ2O Student Note

Electricity Basics

Name	Description (point form)	Unit of Measurement
Voltage		
Current		
Resistance		

Electronics Components


Below are some items and symbols that will be important for working with electronics.

Component Picture	Draw Schematic	Component Name	Brief Description
			
			
			
			
			
			

Appendix C – Activity 2 Resources – Intro to Breadboarding

Resources: The video lesson “TEJ2O A2 - Introduction to Breadboards and Basic Circuits on Tinkercad” is provided to give a basic overview of the Tinkercad Simulator and how to use breadboards and basic components.

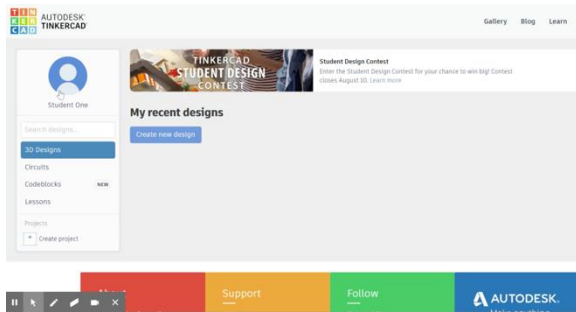Web link: Video – [Introduction to Breadboards and Basic Circuits on Tinkercad](#)




[https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2 - Introduction to Breadboards and Basic Circuits on Tinkercad.mp4](https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2_-_Introduction_to_Breadboards_and_Basic_Circuits_on_Tinkercad.mp4)


A Student Activity Sheet follows to accompany this video.

Section A: Create Basic Circuits on a Breadboard


Circuit #1 – LED and Resistor

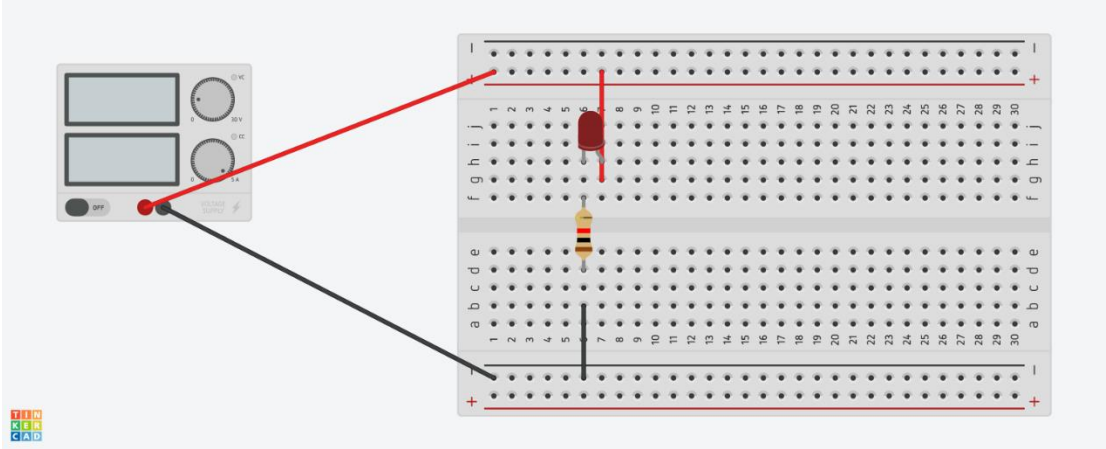

Circuit #2 – Button, LED and Resistor

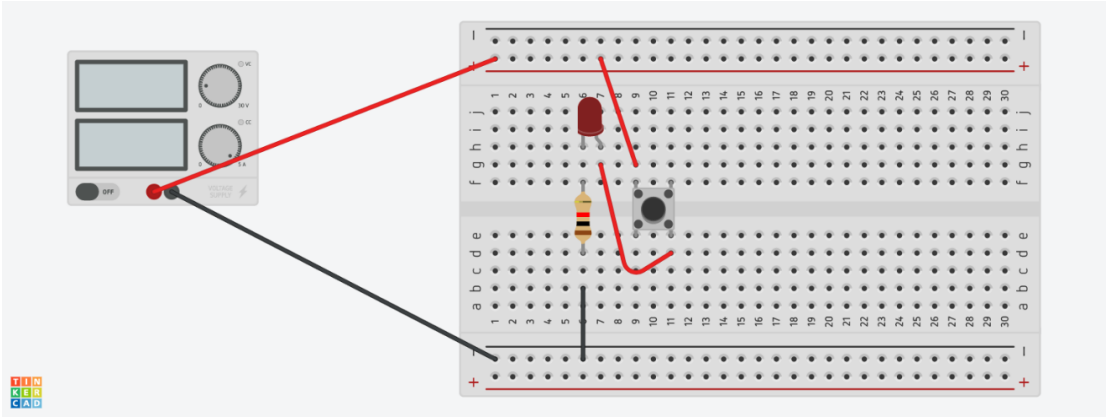


Circuit #3 – Switch, LED and Resistor

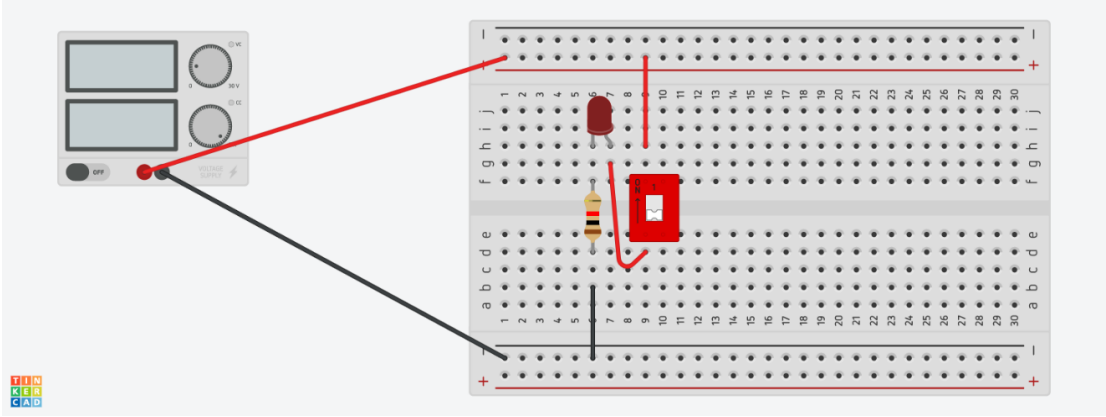

Section B: Draw the Circuit Schematics for Circuits in Section A

Completed Example - Circuit #1:

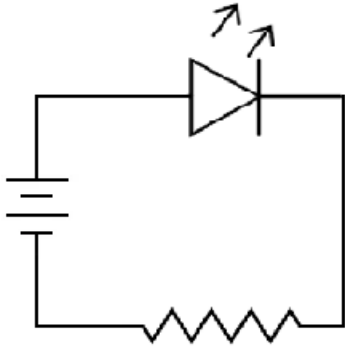*Notice that we are only showing the electronics components not the breadboard we are using for testing.



Circuit #2:

Circuit #3:

Appendix D – Activity 3 Resources - Intro to Boolean Logic and Integrated Circuit Chips

Resources Included:

3a: TEJ2O Activity 3a Intro to Boolean Logic - Teacher.pptx

Web link: ([Teacher PowerPoint Presentation](#))




https://www.octe.ca/application/files/6615/9624/1658/TEJ2O_Activity_3a_Intro_to_Boolean_Logic_-_Teacher.pptx

3b: Intro to Boolean Logic (Student Note and Worksheet on following pages)

3d: TEJ2O Activity 3d Intro to Logic Chips Exploration.pptx

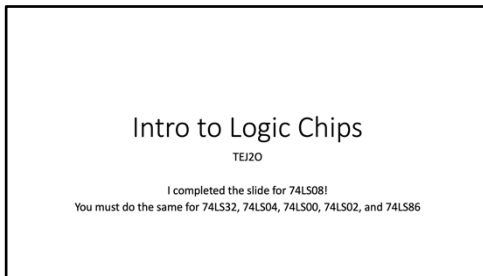Web link: ([Teacher PowerPoint Presentation](#))



https://www.octe.ca/application/files/4915/9624/1744/TEJ2O_Activity_3d_Intro_to_Logic_Chips_Exploration.pptx

3e: Basic Logic IC Chip Layouts (Student Note and Worksheet on following pages)


3f: LogicLY Boolean Assignment (Scaffolding Activity on following pages)

3g: Integrated Circuits on Tinkercad Activity (Student Worksheet on following pages)

3h: Logic Gates and Integrated Circuits Quiz (on following pages)

3i: TEJ2O A3 - AND Integrated Circuit on Tinkercad.mp4

Web link: ([Video](#))

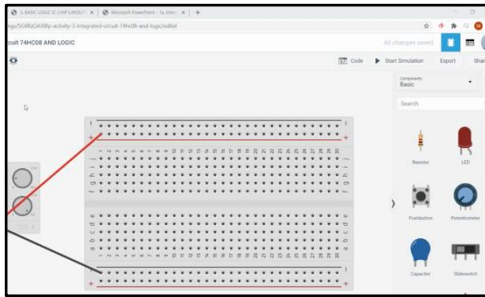

[https://www.octe.ca/application/files/5515/9624/2225/TEJ2O_A3 - AND Integrated Circuit on Tinkercad.mp4](https://www.octe.ca/application/files/5515/9624/2225/TEJ2O_A3_-_AND_Integrated_Circuit_on_Tinkercad.mp4)

Boolean Logic – TEJ2O Student Note and Worksheet

Student Note

Remember that: 1 = _____ or _____ 0 = _____ or _____

Boolean logic is used in almost every aspect of _____ .

In the _____, George _____ developed a new form of algebra, now called Boolean algebra in his honour.

Boolean equations use the _____ number system to provide a very precise way of illustrating the logic of _____ .

Interesting fact: Boolean equations were used _____ !

A gate is where _____ (or _____) flows through. The gate takes the _____ (usually A and/or B) and gives an _____ (Y and/or X).

Schematic	Gate	Symbol	Boolean Equation
	AND		
	OR		
	NOT		
	NOR		
	XOR (EOR)		
	NAND		

Truth Tables

AND		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	

OR		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	

NOT		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	


NOR		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	

XOR (EOR)		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	

NAND		
A (Input)	B (Input)	Y (Output)
0	0	
0	1	
1	0	

Boolean Logic – Worksheet

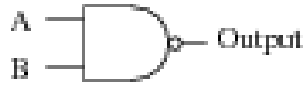1. Identify each of these logic gates by name, and complete their respective truth tables:
**Note: 3 of the gates are NOT in the note but you should be able to use your knowledge to extend your thinking.*




A	B	Output
0	0	
0	1	
1	0	
1	1	

Name: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	

Name: _____

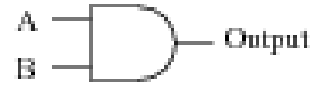

A	B	Output
0	0	
0	1	
1	0	
1	1	

Name: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	

Name: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	

Name: _____



A	Output
0	
1	

Name: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	

Acts Like: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	







Acts Like: _____



A	B	Output
0	0	
0	1	
1	0	
1	1	

Acts Like: _____

Basic Logic IC Chip Layouts – TEJ2O Student Note
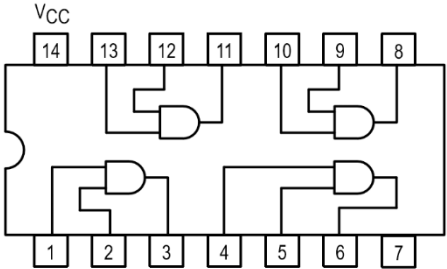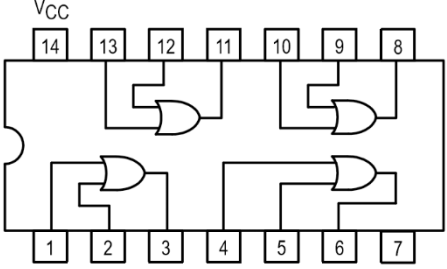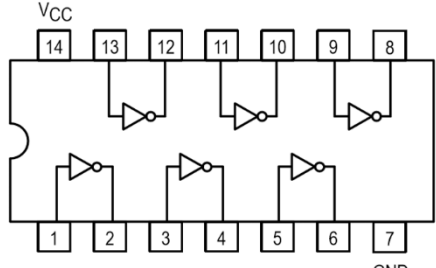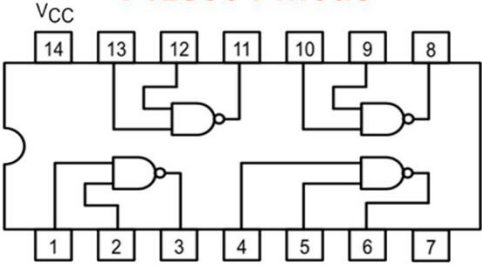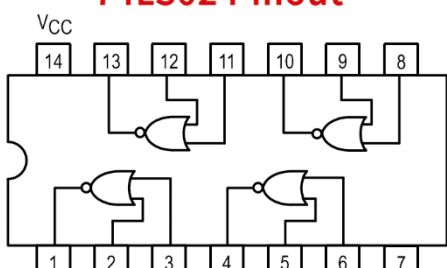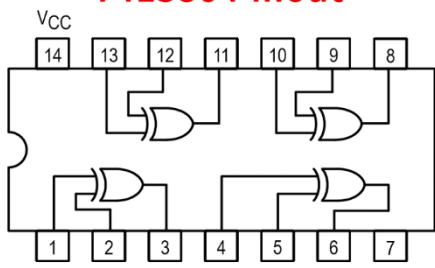
<p>74LS08 (AND CHIP) *aka 74HC08</p> <p>74LS08 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>	<p>74LS32 (OR CHIP) *aka 74HC32</p> <p>74LS32 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>
<p>74LS04 (NOT CHIP) *aka 74HC04</p> <p>74LS04 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>	<p>74LS00 (NAND CHIP) *aka 74HC00</p> <p>74LS00 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>
<p>74LS02 (NOR CHIP) *aka 74HC02</p> <p>74LS02 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>	<p>74LS86 (XOR CHIP) *aka 74HC86</p> <p>74LS86 Pinout</p>  <p>CIRCUITS DIY SIMPLIFYING ELECTRONICS</p>

Please note:


- 1) All chips use pin 14 (top left) for power
- 2) All chips use pin 7 (bottom right) for ground
- 3) All the chips (except NOT) have 4 gates on the chip (*NOT has 6 gates on the chip)
- 4) The NOR chip is reversed (output, input, input)

Experimenting with Logic Gates on Logic.ly – TEJ20

Today we are going to use Logic.ly to experiment with the logic gates we discussed with Boolean Logic. Use the instructions below to create a standard test circuit. You will be removing and adding new GATES for each test circuit.

Step #1 – Go to <https://logic.ly/demo>

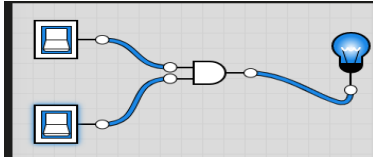Step #2 – Add two toggle switches, a light bulb, and the first gate “AND”. Connect the wires as indicated in the diagram.



Step #3. Click the switch(es) to see the effect on the OUTPUT LIGHT.

Step #4. Take a screen shot (*snipping tool works well*) and SAVE IT as “AND”. Repeat for OR, NAND, NOR, XOR, and NOT (**only one switch needed for NOT*) (6 x 2 marks each = 12 marks)

Step #5 – Complete the table below with all the results as you are doing them. (3 marks)

Gate Type	Sw1	Sw2	Output (On/Off)
AND	Off	Off	
	Off	On	
	On	Off	
	On	On	

Gate Type	Sw1	Sw2	Output (On/Off)
OR	Off	Off	
	Off	On	
	On	Off	
	On	On	

Gate Type	Sw1	Sw2	Output (On/Off)
NAND	Off	Off	
	Off	On	
	On	Off	
	On	On	

Gate Type	Sw1	Sw2	Output (On/Off)
NOR	Off	Off	
	Off	On	
	On	Off	
	On	On	

Gate Type	Sw1	Sw2	Output (On/Off)
XOR	Off	Off	
	Off	On	
	On	Off	
	On	On	

Gate Type	Sw1	Sw2	Output (On/Off)
NOT	Off	N/A	
	On	N/A	


Extension #1: Do the same for XNOR.

Extension #2: Create the following logic gate. $Y = [(A \times B) + C] \times D$

Integrated Circuits: Tinkercad Activity


Step #1: Go to www.tinkercad.com – Login using your course code and nickname

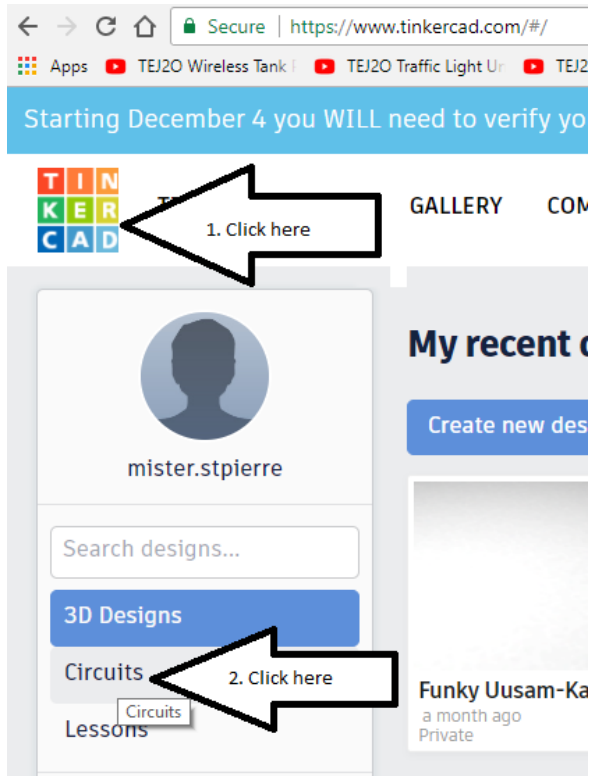Step #2: Go to CIRCUITS (as indicated in screenshot below)



CHIP #1 – SAMPLE CIRCUIT

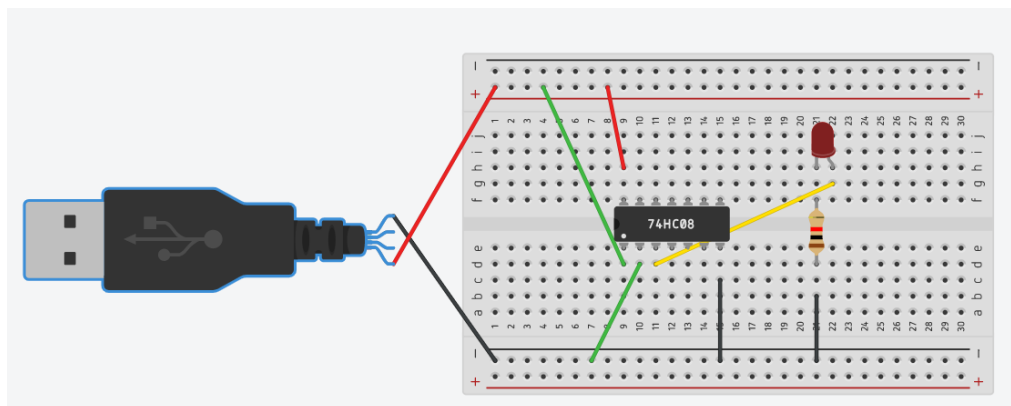Your screenshots should look like this. *NOTE: This shows a value of 1 and 0 in an “AND Gate” so if it was running the LED it should be OFF



Integrated Circuits: Tinkercad Activity Worksheet

Student: _____

CHIP #1 - 74HC08 (we will also refer to it as 74LS08)

Gate Type: _____

Results:

A	B	Y

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS08.png**

CHIP #2 - 74HC32 (we will also refer to it as 74LS32)

Gate Type: _____

Results:

A	B	Y

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS32.png**

CHIP #3 - 74HC04 (we will also refer to it as 74LS04)

**Note that this chip is different*

Gate Type: _____

Results:

A	Y

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS04.png**

CHIP #4 - 74HC00 (we will also refer to it as 74LS00)

Gate Type: _____

Results:

A	B	Y

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS00.png**

CHIP #5 - 74HC02 (we will also refer to it as 74LS02)

*Note that NOR is backwards

Gate Type: _____

Results:

A	B	Y

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS02.png**

CHIP #6 - 74HC86 (we will also refer to it as 74LS86)

Gate Type: _____

Results:

A	B	Y


To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **74LS86.png**

Extension: Advanced Circuit

Results:

A	B	Y	Z

Circuit:

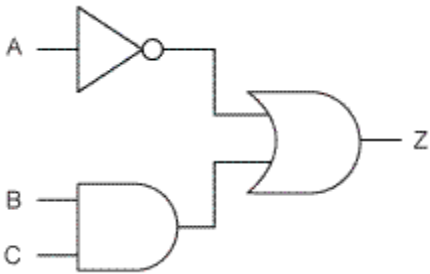

To complete the circuit, take a screen shot (or use snipping tool), paste it into your software of choice and crop it accordingly. Save the image as **ADVANCED.png**

Advanced Circuit Review Questions:

1. Which circuit CHIPS do I need?
2. How many input wires are there in total?
3. What is the final output (Z) if all inputs are HIGH (1)?
4. What is the final output (Z) if all inputs are LOW (0)?
5. Can you confirm the final output (Z) if input A = 1, B = 1 and C is unknown?
6. Can you confirm the final output (Z) if input A = 0, B is unknown, and C is unknown?

Logic Gates and Integrated Circuits - TEJ20 Quiz




Learning Goal: Derive the truth tables of the fundamental logic gates (e.g., AND, OR, NOT, NOR, NAND, XOR);

Student: _____

Total: ____ / 26

1. Complete the truth table for the following gates:


/6

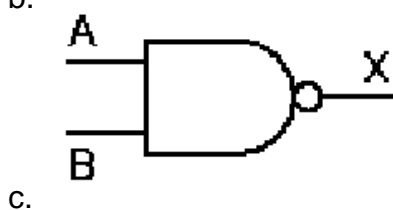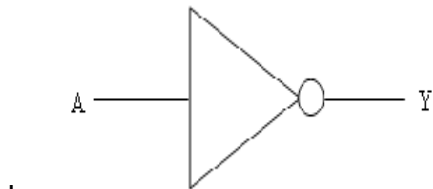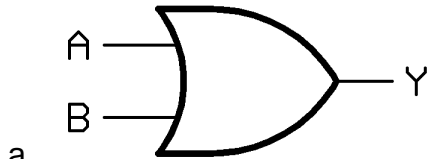

2. Integrated Circuit Chips

a. Identify the 14 pins on the IC below (place number inside the "leg")

/1

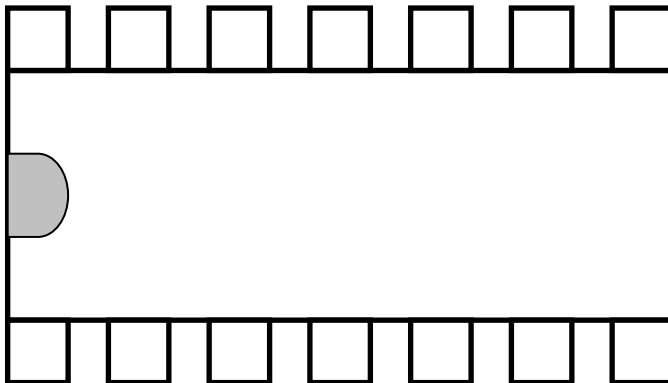

b. Identify: POWER Pin # _____, GROUND Pin # _____

/2

c. Choose one of the chips (circle it) AND, OR, NAND, NOR, NOT, or XOR.
Draw all the gates in the chip above (chip layout)

/4


d. What is the chip number of the chip you chose? 74LS _____

/1

3. For each of the following logic gate circuits you must identify the outputs and the number of Integrated Circuit Chips required to create it on an experimenter breadboard. /12


a. $A = 1, B = 0$ $x = \underline{\hspace{1cm}}, y = \underline{\hspace{1cm}}, z = \underline{\hspace{1cm}}$

of ICs required

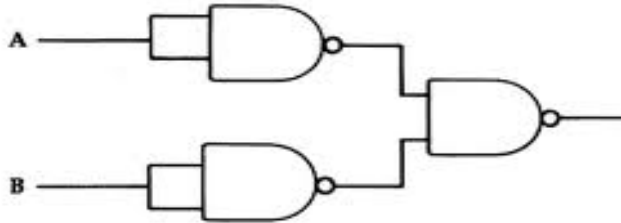


b. $A = 1, B = 1, C = 1, D = 0$ $x = \underline{\hspace{1cm}}, y = \underline{\hspace{1cm}}, z = \underline{\hspace{1cm}}$

of ICs required

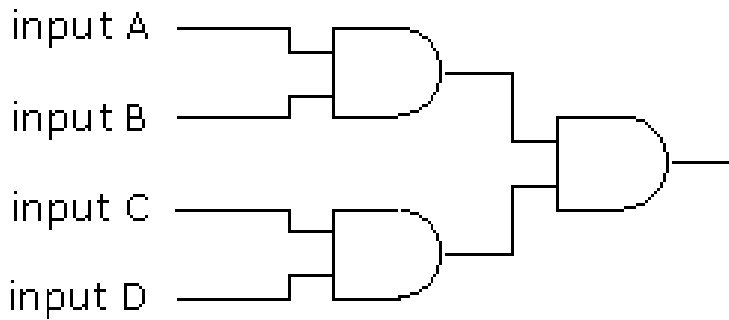

c. $A = 1, B = 0, C = 1$ $x = \underline{\hspace{1cm}}, y = \underline{\hspace{1cm}}, z = \underline{\hspace{1cm}}$

of ICs required

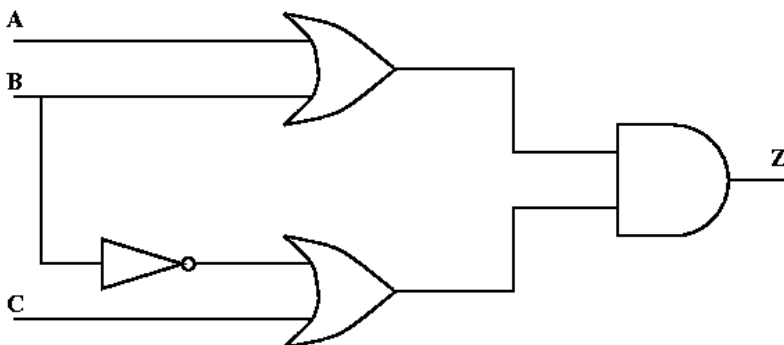


Appendix E – Activity 4 Resources – 555 Timer Circuit

Building a 555 Timer Circuit – TEJ20

In this activity you will be building a circuit that blinks an LED using a polarized capacitor, 555 Timer Chip, and 2 Resistors (R1 = 2K Ohm and R2 = varies see table below).

555 Timer

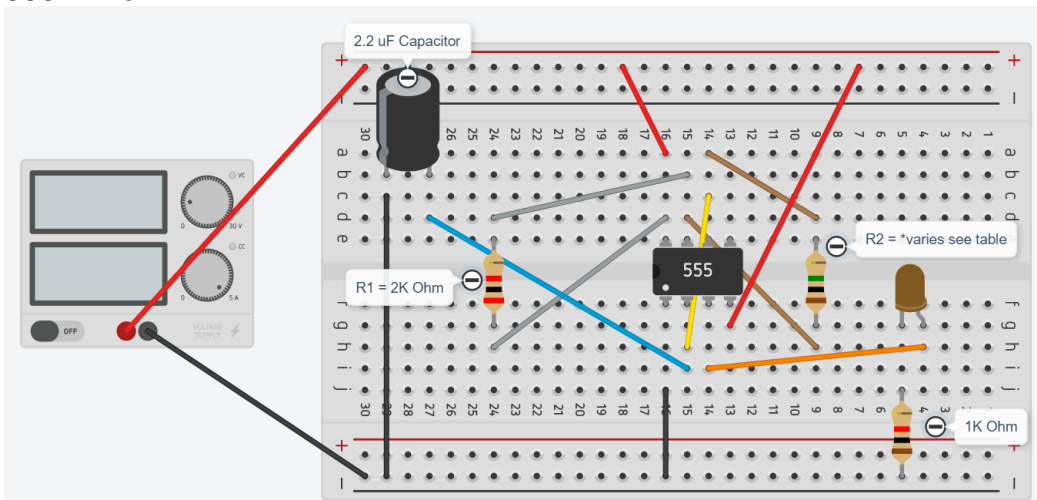

To review reading resistor band values, you can use this online resource:

<https://www.digikey.ca/en/resources/conversion-calculators/conversion-calculator-resistor-color-code-4-band>

4-Band-Code


2%, 5%, 10% 560k Ω \pm 5%

COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)

5-Band-Code

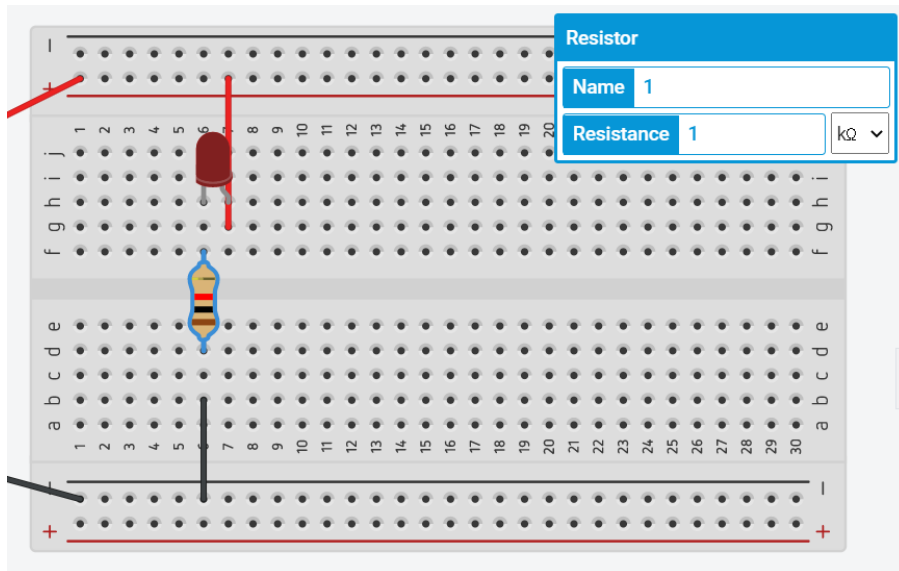0.1%, 0.25%, 0.5%, 1% 237 Ω \pm 1%

Note: Default Resistor Value on TinkerCAD is 1K ohm. You can change the value using a dropdown menu after clicking on the resistor in your circuit.




Try the changing resistor values for R2 in your 555 Timer Circuit (Resistor #2)

R2 Values	4 Band Colour	Speed of Blinking
10K Ohm	brown black orange gold	
100K Ohm	brown black yellow gold	
510K Ohm (first one)	green brown yellow gold	
1M Ohm	brown black green gold	
1.5M Ohm	brown green green gold	

Reflection Questions:


1. What do you notice about the rate of blinking as it relates to the value of R2?
2. If you tried to get your LED to blink ON every 1 second which R2 Value would be best?
3. If you tried to get your LED to blink ON every 5 seconds which R2 Value would be best?
4. If you tried to get your LED to blink ON every 10 seconds which R2 Value would be best?
5. Try changing the value of the Capacitor to 1uF. Notice any change? Why does this change occur?

555 Timer IC Pinout

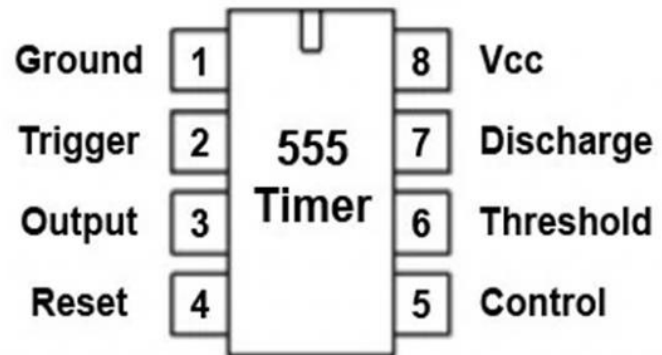


Appendix F – Activity 5 Resources – Seven Segment Display and Decoder Chip

Labelled 7 Segment Pinout for teacher

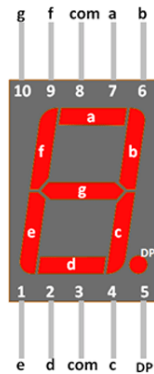


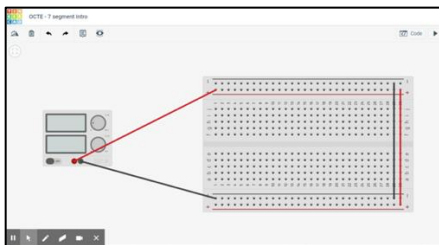Web link: Video – [7 Segment Intro on Tinkercad](#)



[https://www.octe.ca/application/files/3515/9624/2309/TEJ2O_A5a - 7 Segment Intro on Tinkercad.mp4](https://www.octe.ca/application/files/3515/9624/2309/TEJ2O_A5a_-_7_Segment_Intro_on_Tinkercad.mp4)

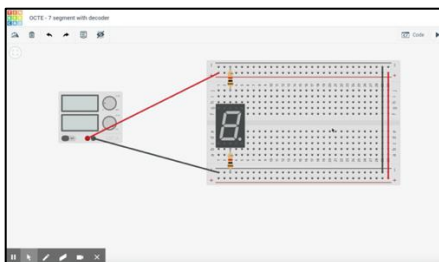Web link: Video – [7 segment with decoder on Tinkercad](#)



[https://www.octe.ca/application/files/6715/9624/2418/TEJ2O_A5b - 7 segment with decoder on Tinkercad.mp4](https://www.octe.ca/application/files/6715/9624/2418/TEJ2O_A5b_-_7_segment_with_decoder_on_Tinkercad.mp4)

Exploring a 7 Segment Display and Decoder Chip – TEJ20


In this activity you will be exploring the 7 Segment Display. These electronic components are made up of 7 “segments” or LEDs which can be used to display digits on an Alarm clock or messages on a scrolling display.

The 7 segments are labeled A through G. The two COMMON pins are #3 and #8. These pins receive power (common anode) or ground (common cathode) depending on the type of 7 segment display. As the segments are tiny LEDs you will use resistors to connect the COM pins to PWR or GND rails.



Label the other 6 segments after completing the circuit below*

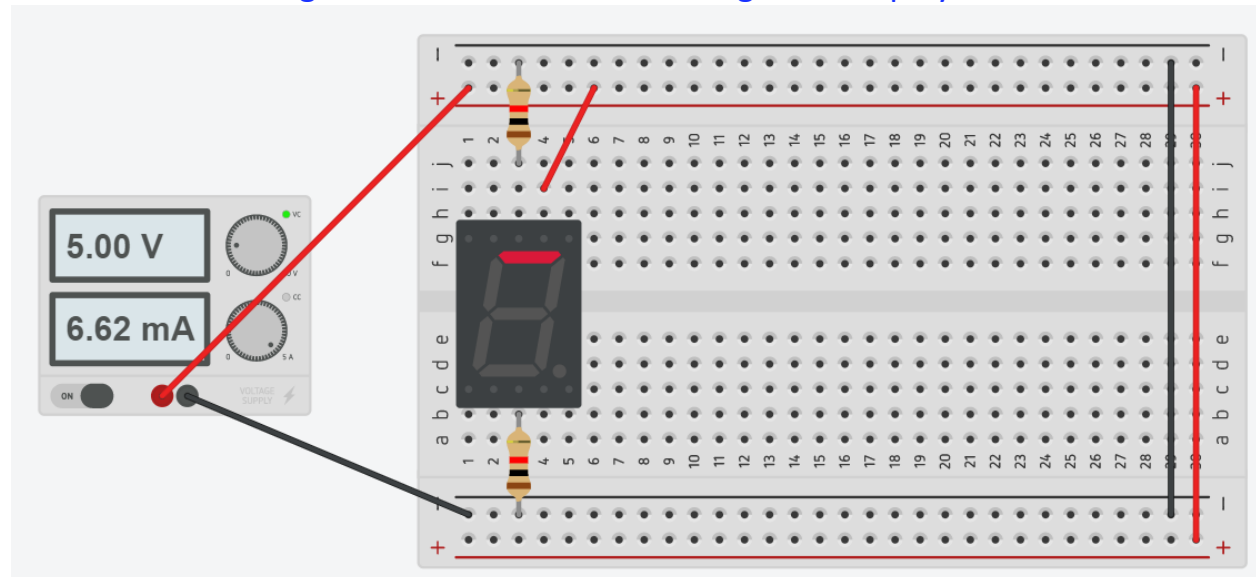Exercise #1 – Wiring a COMMON CATHODE 7 Segment Display




*Notice that the Resistors are connected to GROUND (Common Cathode). In this example “A” PIN is connected to POWER so the “A” Segment is ON. Please label the segments (A through G) on the 7 segment above.

Reflection Questions:


1. Which segments (A through G) need to be ON (PWR) to produce the number ZERO?
2. Which segments (A through G) need to be ON (PWR) to produce the number FIVE?
3. Which segments (A through G) need to be ON (PWR) to produce the number EIGHT?
4. What could the DOT PIN be used for?

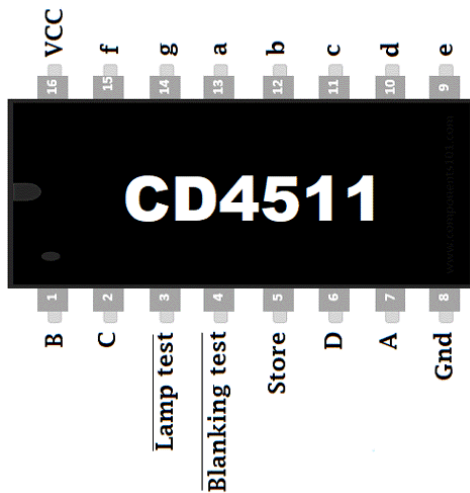Exercise #2 – 7 Segment and Decoder

Now you will drive the 7 segment display with a decoder chip:



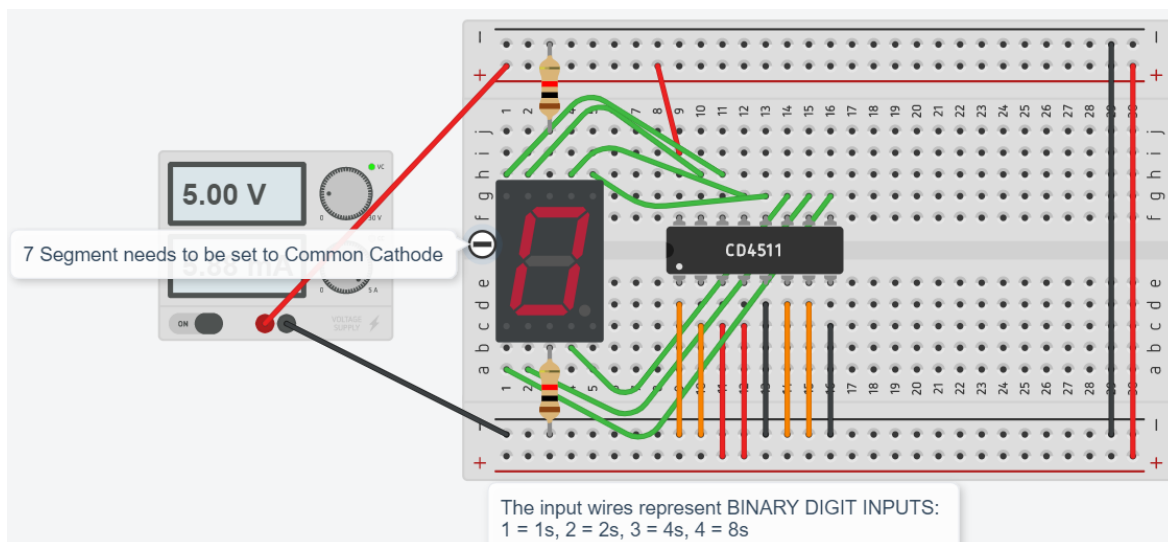Note: While testing this chip we will give PWR to pins #16, #3 and #4 and GND to pin #8 and #5



Use the table below to record the values on 7 segment display based on the input values:


INPUT 4 ($2^3 = 8s$)	INPUT 3 ($2^2 = 4s$)	INPUT 2 ($2^1 = 2s$)	INPUT 1 ($2^0 = 1s$)	7 SEGMENT OUTPUT (DECIMAL DIGIT)
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Reflection Questions:

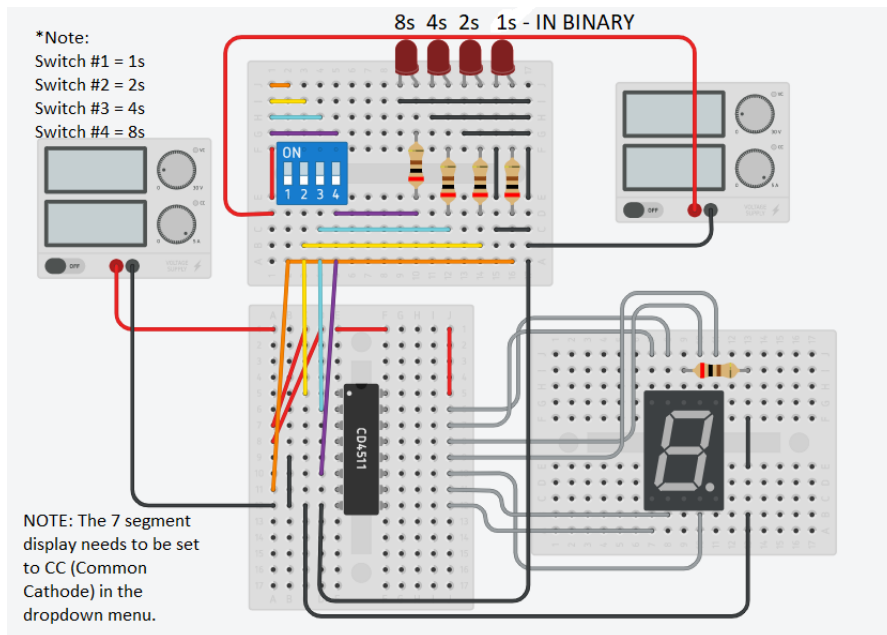1. What do you notice about the "DECIMAL DIGITS" after 1 0 0 1?
2. What should be the DECIMAL VALUE for 1 1 1 1?

Extension:

Try to build this "COMPLEX 7 Segment Display and Decoder"



Appendix G – Activity 6 Resources – Counter Circuit Project

Activity #6 Building a Counter Circuit – TEJ20

In this activity you will be combining all the components to date and creating a counter circuit.



Counter Chip (7493):

OPTION 1: Button Driven Counter Circuit with Reset Button

- Review Activity #2 to see how a button is wired. This button will “DRIVE” the counter chip (7493) on PIN #14.
- QA is connected to “INPUT 1” on CD4511, QB is connected to “INPUT 2”, QC is connected to “INPUT 3”, QD is connected to “INPUT 4”.
- PIN 5 is POWER and PIN 10 is GROUND
- Another button will reset counter to ZERO (both PIN 2 and 3)

OPTION 2: Automated Counter Circuit using 555 Timer

- Review Activity #4 to see how the 555 timer circuit is wired. This circuit will “DRIVE” the counter chip (7493) on PIN #14 (use same pin that blinks the LED in Activity #4)
- Choose an appropriate value for R2 in 555 timer circuit so the blinking is roughly 1 second (accurate time counter).
- QA is connected to “INPUT 1” on CD4511, QB is connected to “INPUT 2”, QC is connected to “INPUT 3”, QD is connected to “INPUT 4”.
- PIN 5 is POWER and PIN 10 is GROUND
- You can add a reset button that will reset counter to ZERO (both PIN 2 and 3)

Counter Circuit Rubric

Learning Goal: safely construct and test electronic circuits (e.g., LED circuit, flasher, timer) using a breadboard to connect discrete components and integrated circuits			
Level 1	Level 2	Level 3	Level 4
Counter circuit design does not incorporate all required components	Counter circuit design includes most required components	Counter circuit design is good with minor errors.	Counter circuit design incorporates all required components and complete the task of counting (either automated with 555 or using 2 buttons)

Counter Circuit Troubleshooting Log:


Issues/Problem	Attempted Solutions	Final Solution
Example: 7 Segment Not Lighting up	*Checked Common Ground Connections, watched teacher video a second time	*Realized that I didn't change 7 segment to "Common Cathode"

Counter Circuit Project Reflection


What I Knew about Electronics (PRE-PROJECT)	What I Want(ed) to Know (DURING)	What I Learned (POST-PROJECT)

Counter Circuit Project Solutions

OPTION 1: Button Driven Counter Circuit with Reset Button

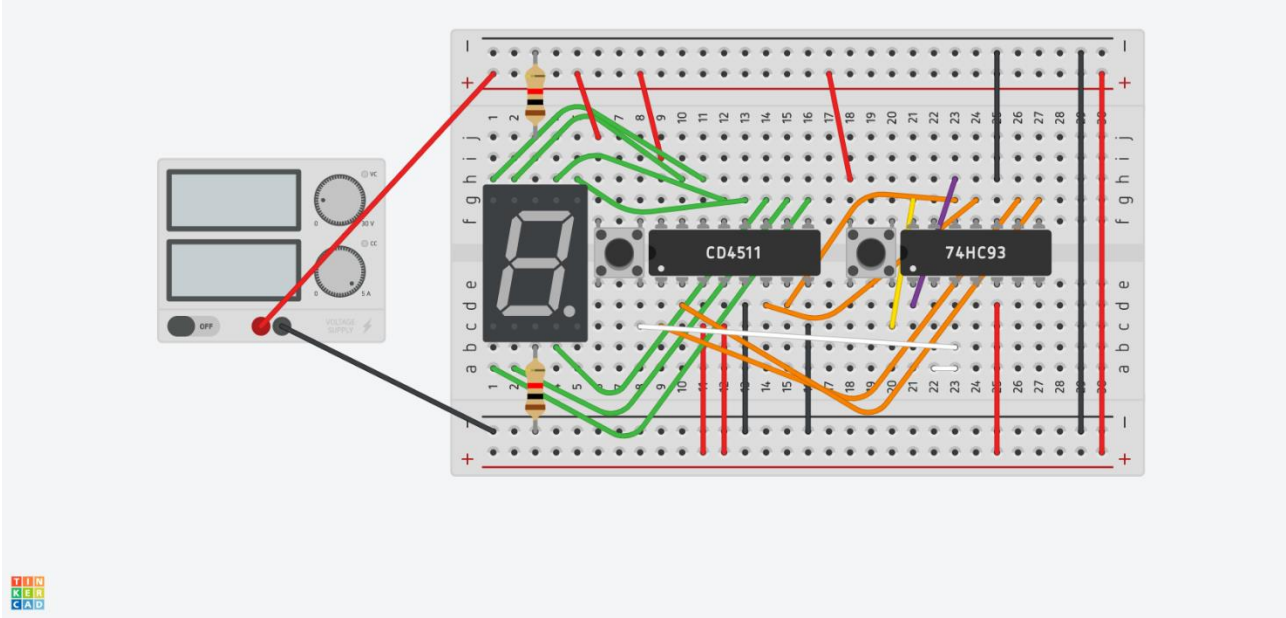

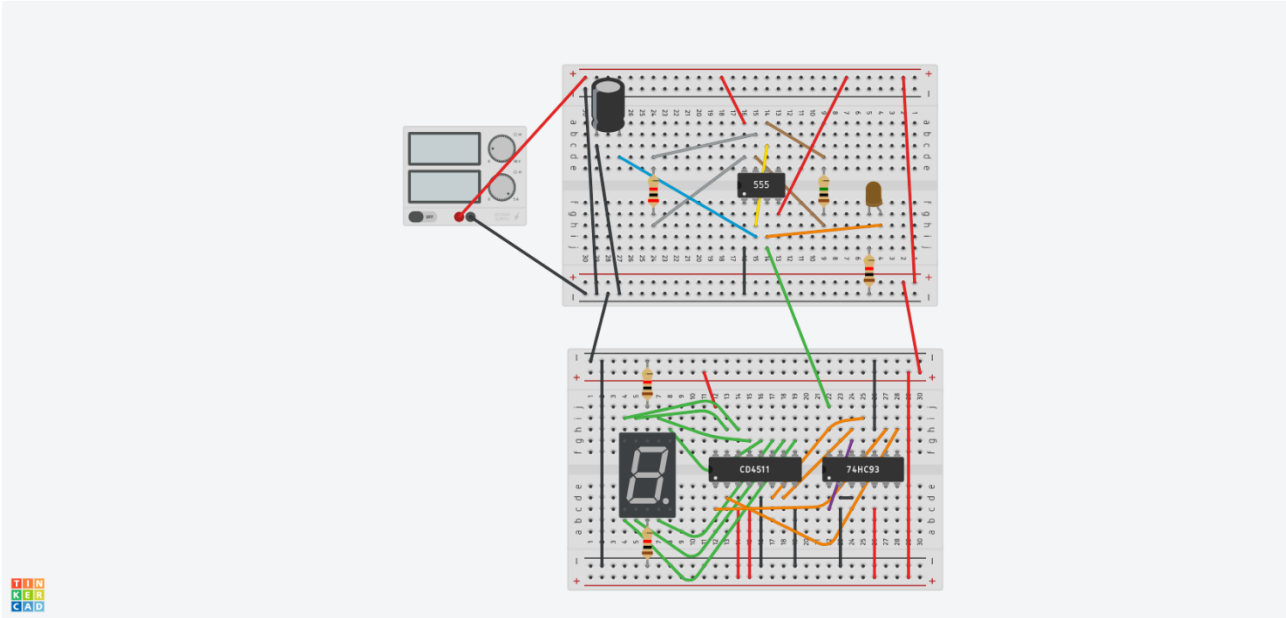OPTION 2: Automated Counter Circuit using 555 Timer



References

4 Band Resistor Color Code Calculator Chart (Image), 2020

<https://www.digikey.ca/en/resources/conversion-calculators/conversion-calculator-resistor-color-code-4-band>

7 Segment Display Pinout (Image), 2020 <https://components101.com/7-segment-display-pinout-working-datasheet>

7 Segment Intro on Tinkercad (Video), 2020

https://www.octe.ca/application/files/3515/9624/2309/TEJ2O_A5a_-_7_Segment_Intro_on_Tinkercad.mp4

7 Segment with Decoder on Tinkercad (Video), 2020

https://www.octe.ca/application/files/6715/9624/2418/TEJ2O_A5b_-_7_segment_with_decoder_on_Tinkercad.mp4

21st Century Competencies: Foundation Document for Discussion. Phase 1: Towards Defining 21st Century Competencies for Ontario, Winter 2016 Edition, 2016

http://www.edugains.ca/resources21CL/About21stCentury/21CL_21stCenturyCompetencies.pdf

74LS00 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls00-quad-two-input-nand-gate-datasheet/>

74LS02 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls02-quad-two-input-nor-gate-datasheet/>

74LS04 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls04-hex-inverter-ic-not-gate-ic-datasheet/>

74LS08 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls08-quadruple-two-input-and-gate-datasheet/>

74LS32 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls32-quad-2-input-or-logic-gate-ic-datasheet/>

74LS86 Chip Pinout (Image), 2020 <https://circuits-diy.com/74ls86-quad-2-input-exclusive-or-xor-gate-ic-datasheet/>

555 Timer IC Chip Pinout (Image), 2020 <https://circuits-diy.com/dark-detector-circuit-using-ldr-and-555-timer/>

AND Integrated Circuit on Tinkercad (Video), 2020

https://www.octe.ca/application/files/5515/9624/2225/TEJ2O_A3_-_AND_Integrated_Circuit_on_Tinkercad.mp4

Capacitor (Image), 2020 <https://www.digikey.com/product-detail/en/rubycon/16ZLJ470MTA8X11-5/1189-1549-1-ND/3134505>

Course Codes for Emphasis courses in the Revised Curriculum: Technological Education, Grades 11 and 12, 2009
<http://www.edu.gov.on.ca/eng/curriculum/secondary/techedemphasiscourses.pdf>

Diode (Image), 2020 <https://www.digikey.com/product-detail/en/smc-diode-solutions/1N4004TA/1N4004TASMC-ND/5992911>

DIP Switch (Image), 2020 <https://www.digikey.com/product-detail/en/cui-devices/DS01-254-S-01BE/2223-DS01-254-S-01BE-ND/11310868>

Growing Success: Assessment, Evaluation, and Reporting in Ontario Schools, First Edition, Covering Grades 1 to 12, 2010
www.edu.gov.on.ca/eng/policyfunding/growSuccess.pdf

Intro to Boolean Logic (PowerPoint Presentation), 2020
https://www.octe.ca/application/files/6615/9624/1658/TEJ2O_Activity_3a_Intro_to_Boolean_Logic_-_Teacher.pptx

Intro to Logic Chips (PowerPoint Presentation), 2020
https://www.octe.ca/application/files/4915/9624/1744/TEJ2O_Activity_3d_Intro_to_Logic_Chips_Exploration.pptx

Introduction to Breadboards and Basic Circuits on Tinkercad (Video), 2020
https://www.octe.ca/application/files/9215/9624/2124/TEJ2O_A2_-_Introduction_to_Breadboards_and_Basic_Circuits_on_Tinkercad.mp4

Learning for All – A Guide to Effective Assessment and Instruction for All Students, Kindergarten to Grade 12, 2013
<http://www.edu.gov.on.ca/eng/general/elemsec/speced/LearningforAll2013.pdf>

LED (Image), 2020 <https://www.digikey.com/product-detail/en/broadcom-limited/HLMP-AB75-WXBDD/516-3974-3-ND/2756797>

Logically Digital Logic Simulator (Website), 2020 <https://logic.ly/demo>

Momentary Button (Image), 2020 <https://www.digikey.com/product-detail/en/cit-relay-and-switch/CT1103AF180/2449-CT1103AF180-ND/12502982>

Resistor (Image), 2020 <https://www.digikey.com/product-detail/en/ohmite/OX102KE/OX102KE-ND/823904>

The Differentiated Instruction Scrapbook
<http://www.edugains.ca/resourcesDI/EducatorsPackages/DIEducatorsPackage2010/2010DIScrapbook.pdf>

The Ontario Curriculum, Grades 9 and 10: Technological Education, 2009 (revised)
<http://www.edu.gov.on.ca/eng/curriculum/secondary/teched910curr09.pdf>

The Ontario Curriculum, Grades 11 and 12: Technological Education, 2009 (revised)
<http://www.edu.gov.on.ca/eng/curriculum/secondary/2009teched1112curr.pdf>

Tinkercad (Website), 2020 <https://www.tinkercad.com/>